

Memory




- Address n bits, 2^n locations in memory
- Memory stores m bits, $m * 2^n$ storage

RAM

- fast, limited, volatile, no program code
 - SRAM (static - retains value as long as have power)
 - DRAM (dynamic - capacitor; slowly lose info unless refreshed)



MOSFET

   - 3 terminals: Source, Gate, Drain
 - Gate voltage $> V_{th}$, Source connected to Drain
 - Gate voltage $\leq V_{th}$, transistor is open switch



SRAM Cell

  
- 2 inverters connected in a loop
 - 2 access transistors control reading and writing the cell
 - WL is enable
 - READ $WL = 1$, data in cell will appear on bitline BL
 - WRITE $WL = 1$, drive BL and \overline{BL} to strong values, when $WL \rightarrow 0$, value retained



SRAM Organization

- SRAM with 8 locations, 6 bits each
- 3 bit address one-hot decoded to 8 bit values
 - 1 wordline is selected
- Drivers (top) push current on BL and NBL

 - sense amplifier at bottom boosts weak current from each cell



DRAM

- stores value using 1C
 - sufficient charge = 1, else 0
 - 1 access transistor
- WRITE - set BL to Vdd/GND, activate WL - charge/discharge the capacitor
- READ - pre-charge BL to **Vdd/2** and activate WL
 - if C stored Vdd, BL voltage increase
 - If C stored GND, BL voltage decrease
 - sense amplifier boosts this small difference

DRAM READ




- destructive
 - needs write back after read
- DRAM needs recharge (cells lose charge overtime)
 - DRAM self refresh - re-write values to capacitors so they don't lose all their charge
 - few ms
- additional circuitry for *self refresh* and *writing back read values*
- 20x denser than SRAM but 10x slower

ROM



- meant for program code - shouldn't change once dev in use
 - used to be program once by manufacturer and cannot change

Flash Cell

   - FGFET (floating-gate transistor)
 - like MOSFET, but with 2 gates
- floating gate layer is electrically insulated
 - any electron on this gate are trapped; charge takes month to leak
- floating gate blocks usual FET operation
 - if charge exists on FG, prevents current flow from Src to Drain even if control gate voltage $> V_t$



- A charged floating gate (electrons trapped) represents one binary state (typically a "0")
- An uncharged floating gate represents the other state (typically a "1")
- READ
 - set both Src and Gate to Vdd/1
 - no charge on FG, regular MOSFET and read 1
 - yes charge on FG, read 0 at drain
 - *cells with charge store 0*
- Changing val of cell
 - to drain a charged cell (i.e. change a 0 to a 1), need to erase the cell
 - process is slow

  

Flash Blocks & Wearout

- to speed up erasing, cells are grouped into blocks, erased together
 - block size 8KB ~ 256KB
 - when we do write, single bit 0→1, we must erase the **entire block** and write it all again ?????
- flash memory suffers from wearout if used too much
 - write to a cell *too many* times, it no longer stores charge

NAND NOR Flash



- 2 ways to arrange FGFET
 - connect in **parallel NOR flash**
 - supports fast read, slow writes
 - byte-granularity accesses
 - good for code (supports execute in place)
 - connect in **series NAND flash**
 - slow reads, fast writes

- higher density than NOR
- better for storage (USB drives)

	NOR	NAND
Read	0.1 μ S	30 μ S
Erase	500 ms	3.5 ms
Block size	64KB to 256KB	8KB to 32KB
Bad blocks	0%	~1-2%
Capacity	64MB - 2GB	1GB - 16GB
Cost	\$\$	\$
Erase cycles	$10^4 - 10^5$	$10^5 - 10^6$

Other ROM

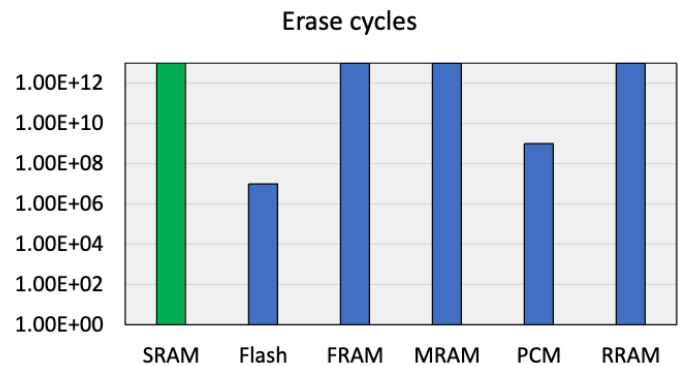 - non volatile memory
 - ferroelectric ram, magnetoresistive RAM, PCM...



Memory	Location	Latency	Small	Medium	Large
SRAM	On-chip	1 – 10 ns	1 KB – 256 KB	256 KB – 1 MB	1 MB – 16 MB
NOR Flash	On-chip	100 ns			
NOR Flash	Off-chip	250 ns			
NAND Flash	Off-chip	10,000 ns	2 MB – 16 MB	16 MB - 256 MB	256 MB – 64 GB
DRAM	Off-chip	100 ns	-	32 MB – 1 GB	1 GB – 16 GB